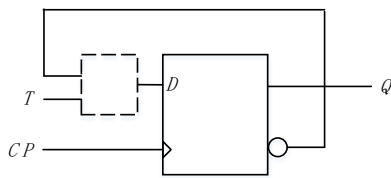



Chapter Five: Flip-Flop

1. **True or False.** To convert a D flip-flop to a T flip-flop, the gate that is connected with the D should be an (AND gate).



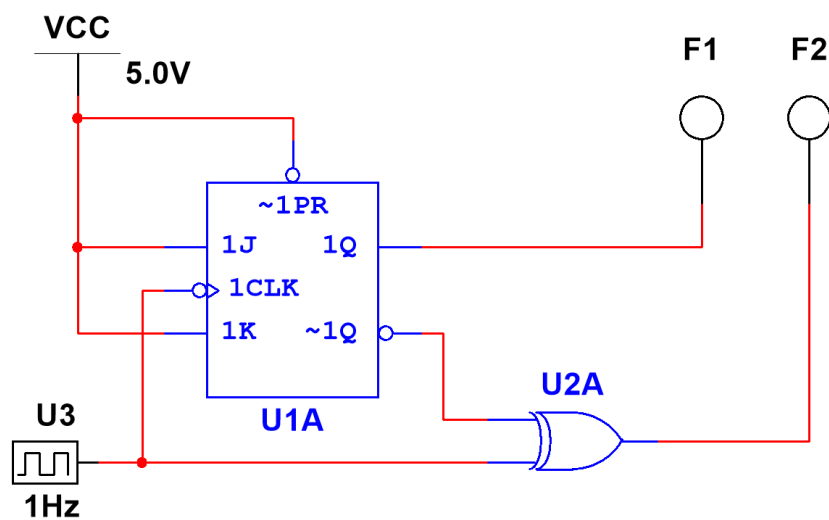2. Draw the waveforms.

Analyze the synchronous sequential logic circuit shown in the following figure which contains a JK flip-flop and one XOR gate.



Suppose the initial state of F1 is 1, please sketch the output waveforms.

