

Part 2. Write your answers in the blanks.

1. In the twisted counter composed of $2n$ flip-flops, there are at most () effective states.

1. 用 $2n$ 个触发器组成的扭环计数器最多有 () 个有效状态。